

MISR UNIVERSITY FOR SCIENCE AND TECHNOLOGY
COLLEGE OF ENGINEERING
MECHATRONICS DEPARTMENT



MTE 405 SENSORS AND MEASUREMENTS

LAB 2 – SPRING 2020

Lab 1

Goals Of The Lab

Introduction to Sensors and Signal Conditioning with Virtual Prototyping



Introduction to
temperature sensors



Spreading signal output
range


Lab 2

Sensing Temperature

Analog sensors

Learning outcome

- LM35 characteristics.
- Simulation of LM35 on Proteus.
- Improving LM35 range.
- Practical implementation

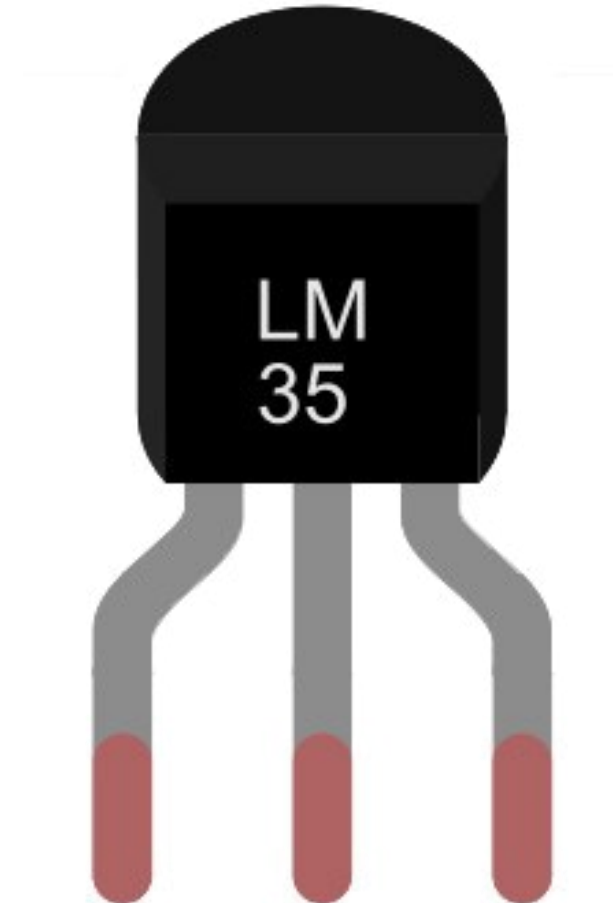


Lab 2

Sensing Temperature

LM35

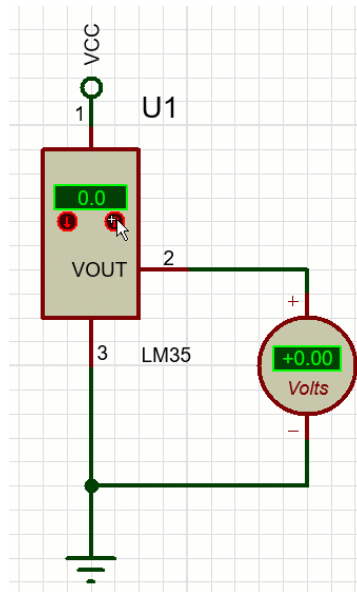
- ✓ Voltage supply : 4 – 30 V
- ✓ Sensitivity : 10 mV / °C
- ✓ Useful range : 2 – 150 °C
- ✓ Less than 50 μ A




LM35 Precision Centigrade

1 Features

- Calibrated Directly in Celsius (Centigrade)
- Linear + 10-mV/°C Scale Factor
- 0.5°C Ensured Accuracy (at 25°C)
- Rated for Full -55°C to 150°C Range
- Suitable for Remote Applications
- Low-Cost Due to Wafer-Level Trimming
- Operates From 4 V to 30 V
- Less Than 60- μ A Current Drain
- Low Self-Heating, 0.08°C in Still Air
- Non-Linearity Only $\pm 1/4^\circ\text{C}$ Typical
- Low-Impedance Output, 0.1 Ω for 1-mA Load

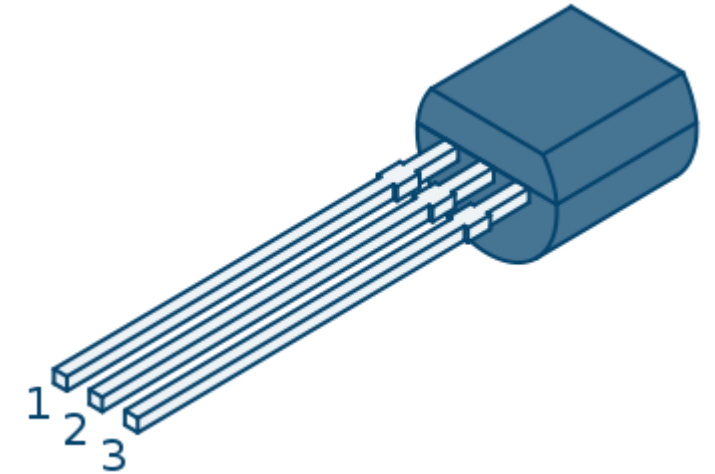


1. Vcc
2. Output
3. Gnd

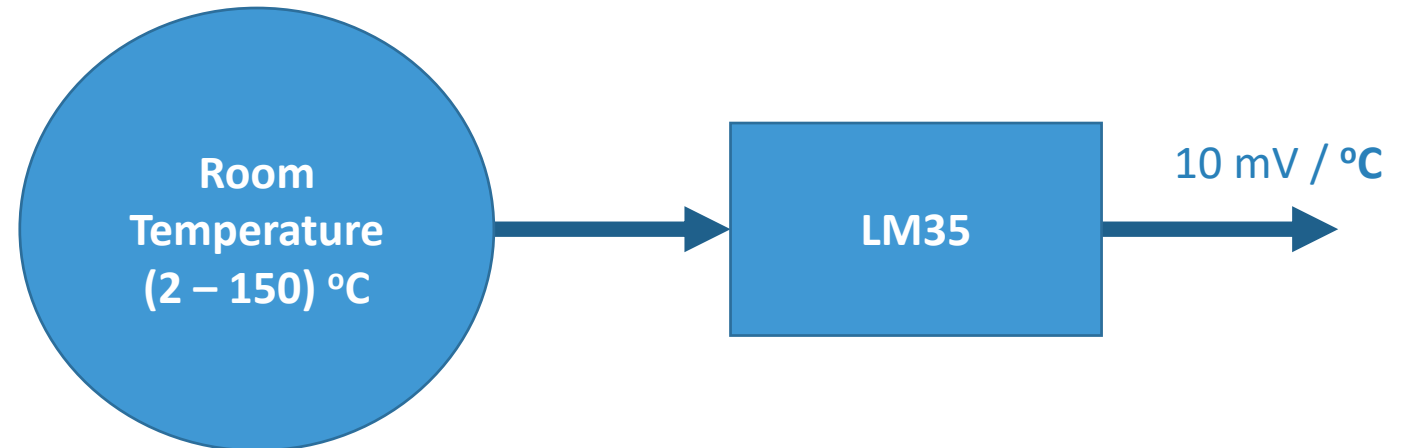

Sensing Temperature

LM35

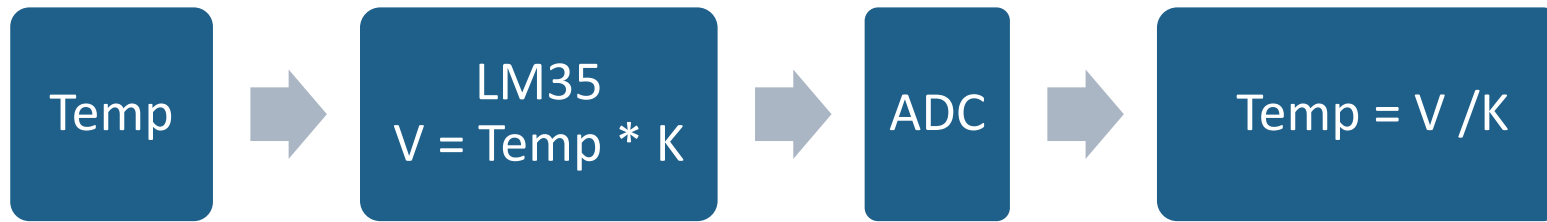


Acquisition Transfer Function

Where

K Conversion factor

And
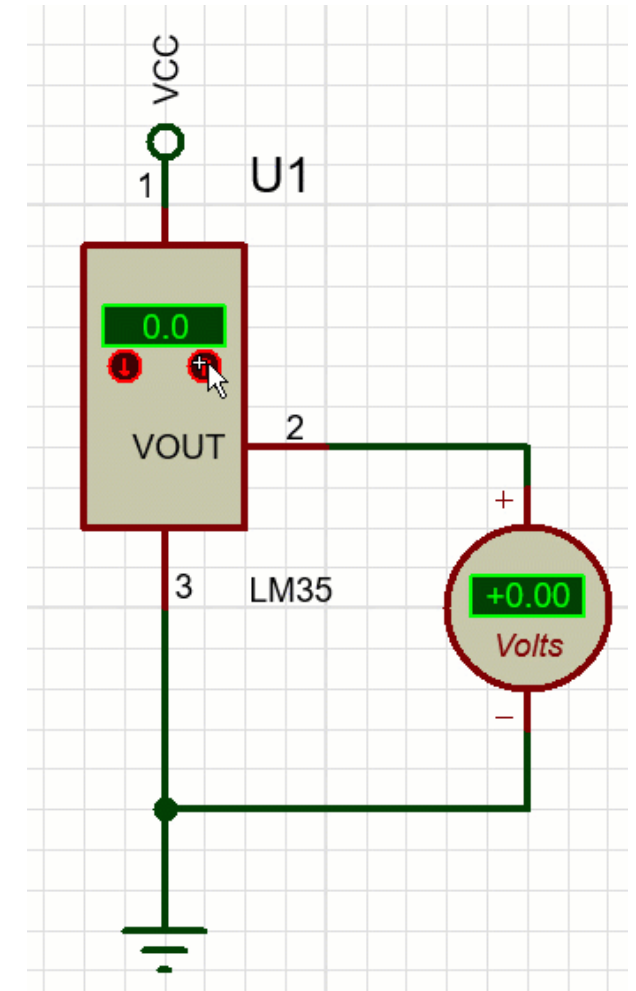
$$K = (10 \text{ mV} / 1000 \text{ mV})$$




Improving Sensor Range

Case Study

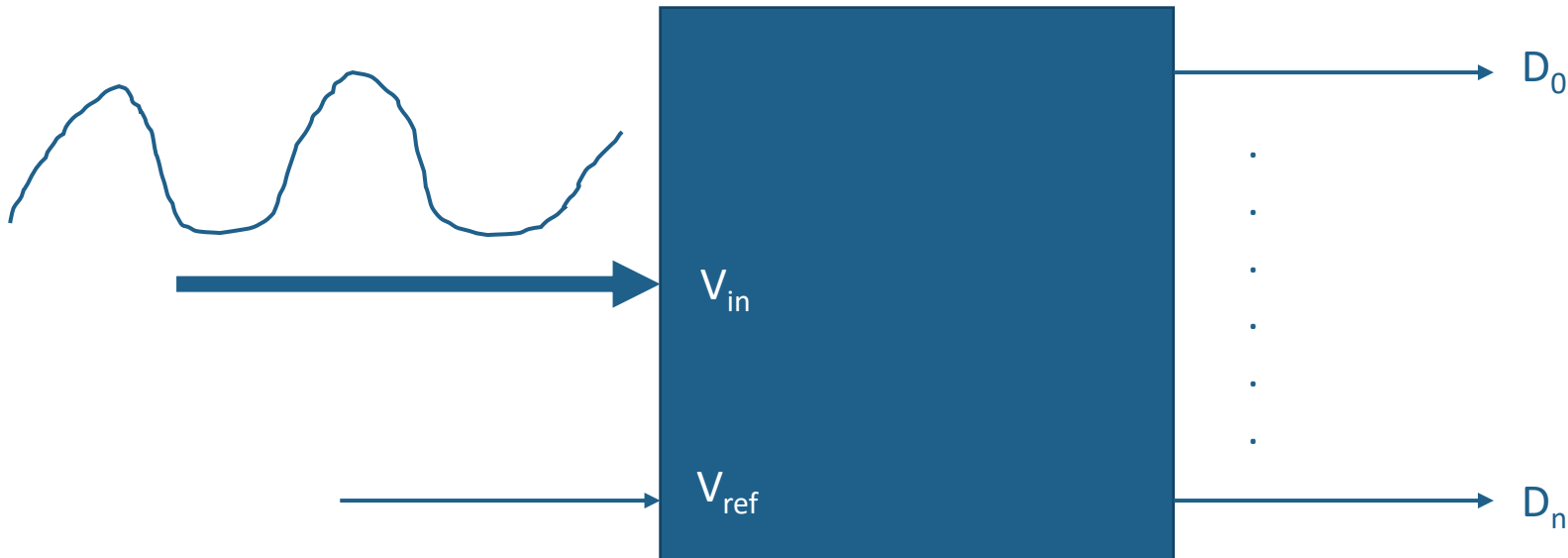PROBLEM DEFINITION

- You wish to build an embedded system for monitoring **temperature** using LM35.
- Your temperature **range** is expected to vary from **5 – 45 °C**
- You have **built-in 10-bit ADC** with **reference** voltage of **5V (resolution?)**.
- You are **assigned** to **improve the voltage range of LM35** to match ADC input voltage range for the input temperature range



$$ADC \text{ Resolution} = \frac{V_{ref}}{2^n}$$




$$Digital \text{ Value} = \frac{V_{in}}{ADC \text{ Resolution} - \mathbf{1}}$$

Improving Sensor Range

Case Study

FOR LM35

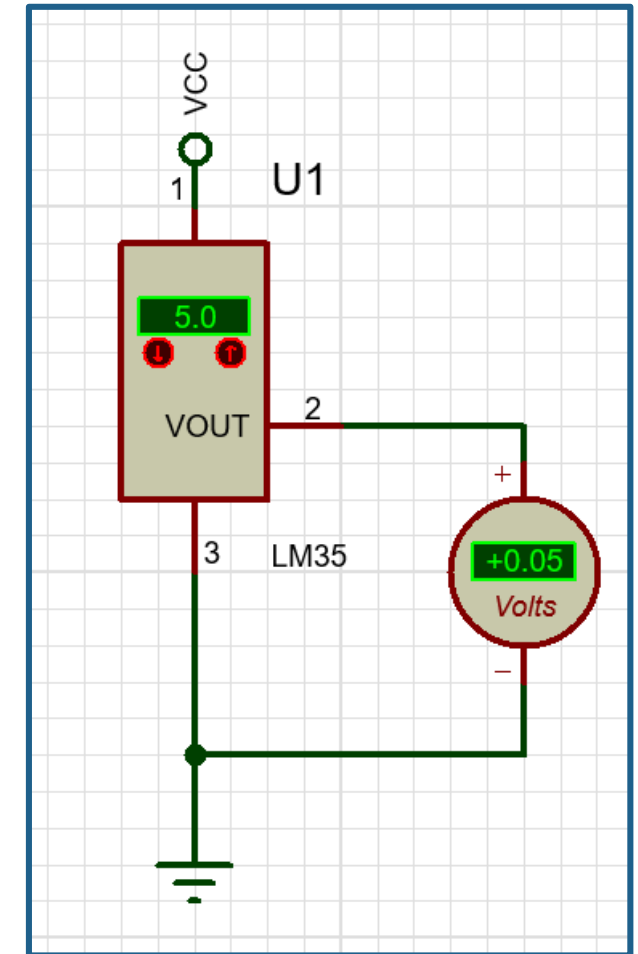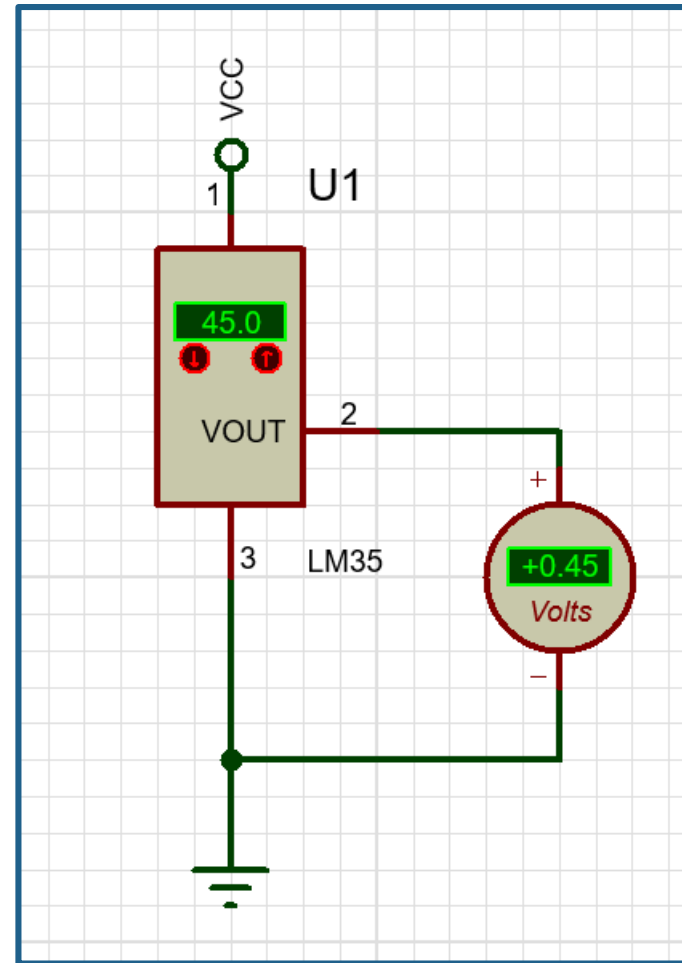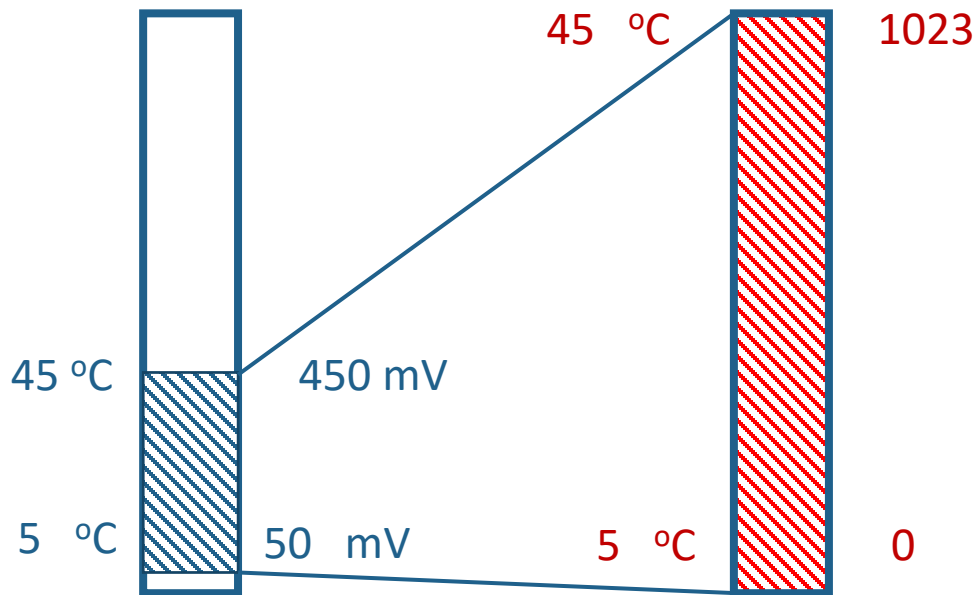- At 5 °C $\rightarrow V_{\text{lm35}} = 5 \times 10\text{mV} = 50 \text{ mV}$
- At 45 °C $\rightarrow V_{\text{lm35}} = 45 \times 10\text{mV} = 450 \text{ mV}$



What is the loss percentage in ADC range?

Lab 2

Improving Sensor Range

Case Study

FOR LM35


- At 5 °C $\rightarrow V_{\text{lm35}} = 5 \cdot 10\text{mV} = 50 \text{ mV}$
- At 45 °C $\rightarrow V_{\text{lm35}} = 45 \cdot 10\text{mV} = 450 \text{ mV}$

STEP 1 (Range Mapping)

- 50 mV $\rightarrow 0\text{V}$ (ADC Vin min)
- 450 mV $\rightarrow 5\text{V}$ (ADC Vin max) = V_{ref}

STEP 2 (Shifting)

- 50 mV $\rightarrow 0\text{V}$ (Voltage Divider + **Buffer** “why?”)

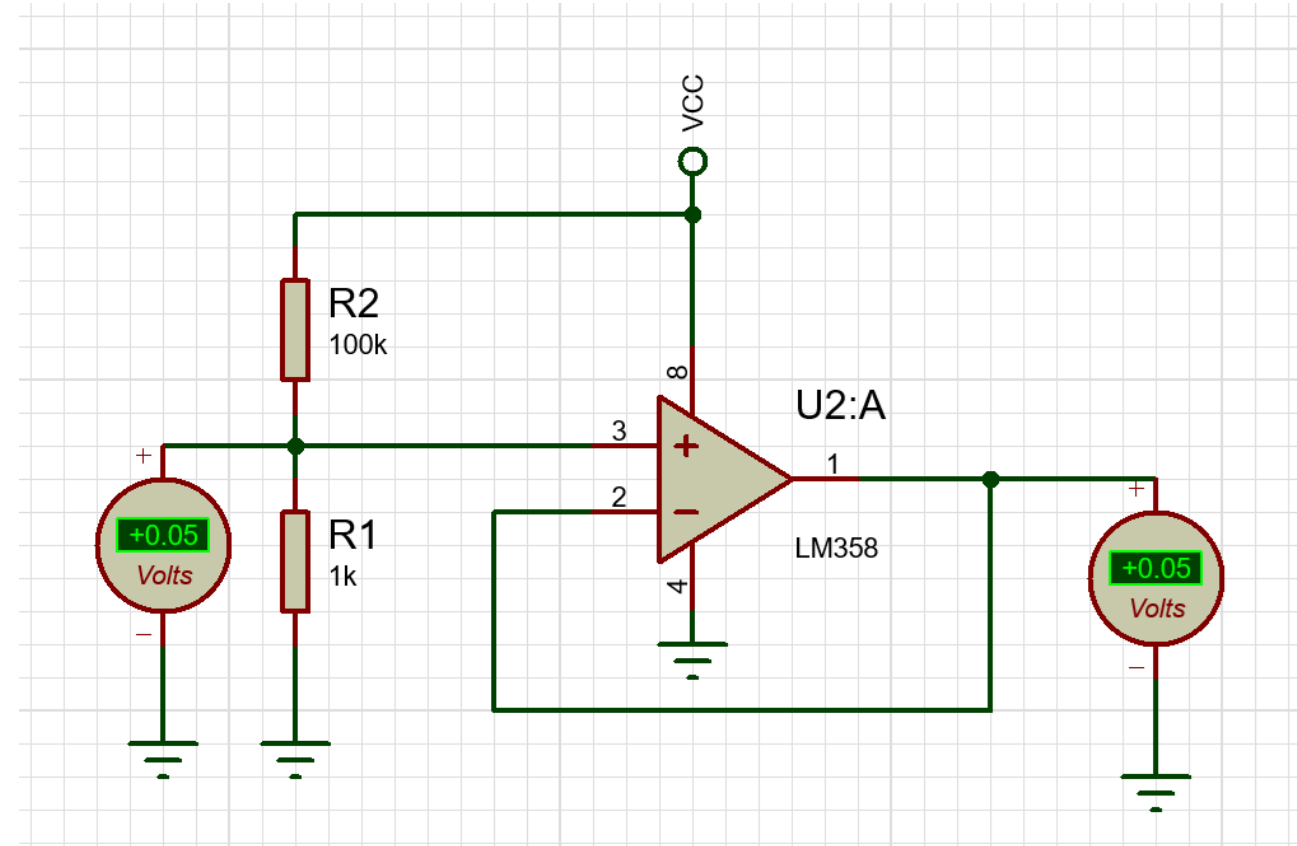

Lab 2

Improving Sensor Range

Case Study


$$V(offset) = 5 * \frac{100k}{1k} = 50 \text{ mV}$$

$$V(out) = V_{LM \rightarrow 50^{\circ}C} - V(offset) = 0V(\text{Theoretical})$$

$$V(out) = 0.05 - 0.05 = 0V + \text{Amplifier DC offset}$$

STEP 2 (Shifting)

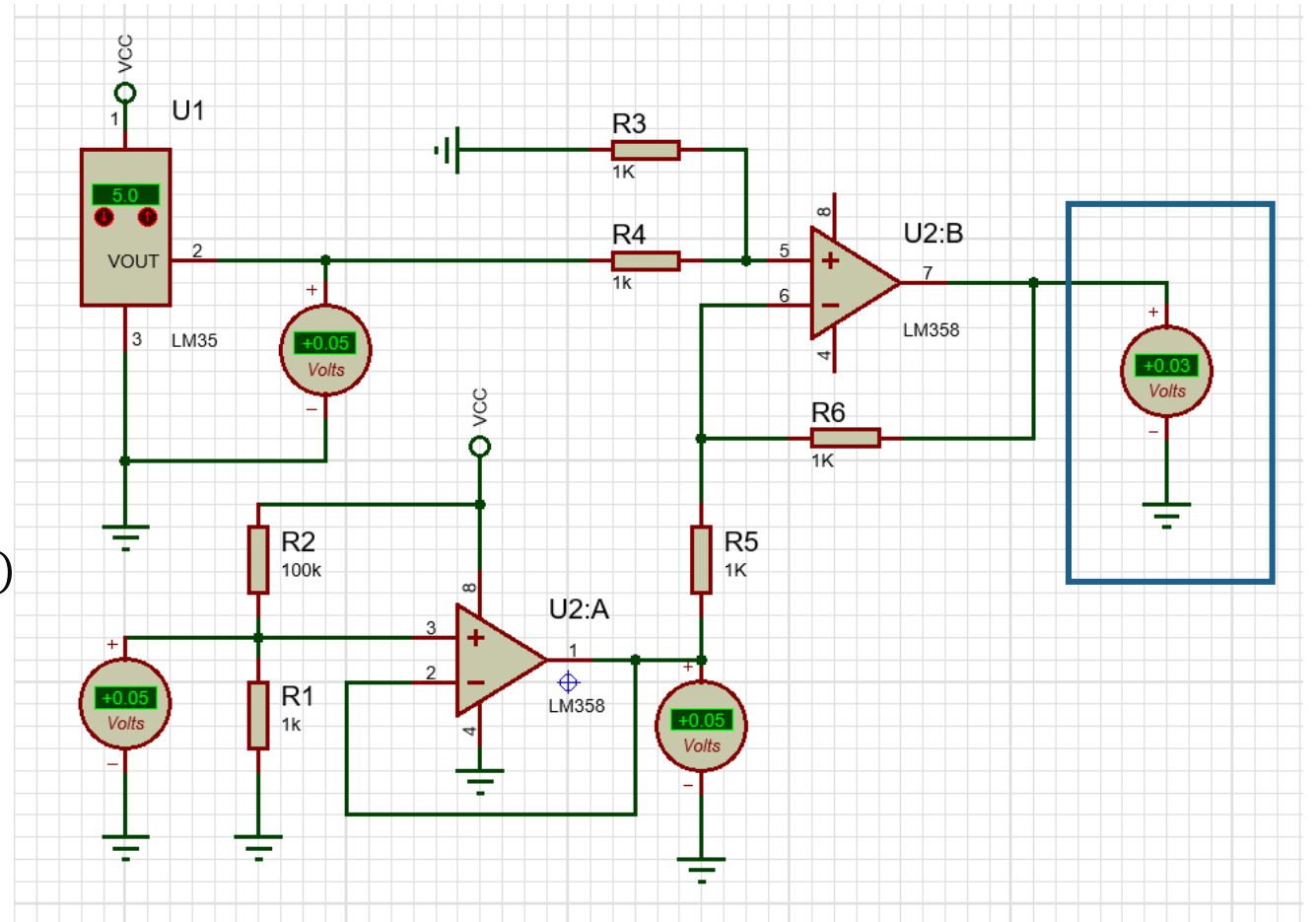- 50 mV → 0V (Voltage Divider + Buffer
“why?”)



Read about **amplifier DC offset**

Lab 2

Improving Sensor Range

Case Study

After min voltage removal


$$V(450) = 0.45 - 0.05 = 0.$$

Gain

$$G = \frac{5}{0.4} = 12.5$$

STEP 3 (Amplification)

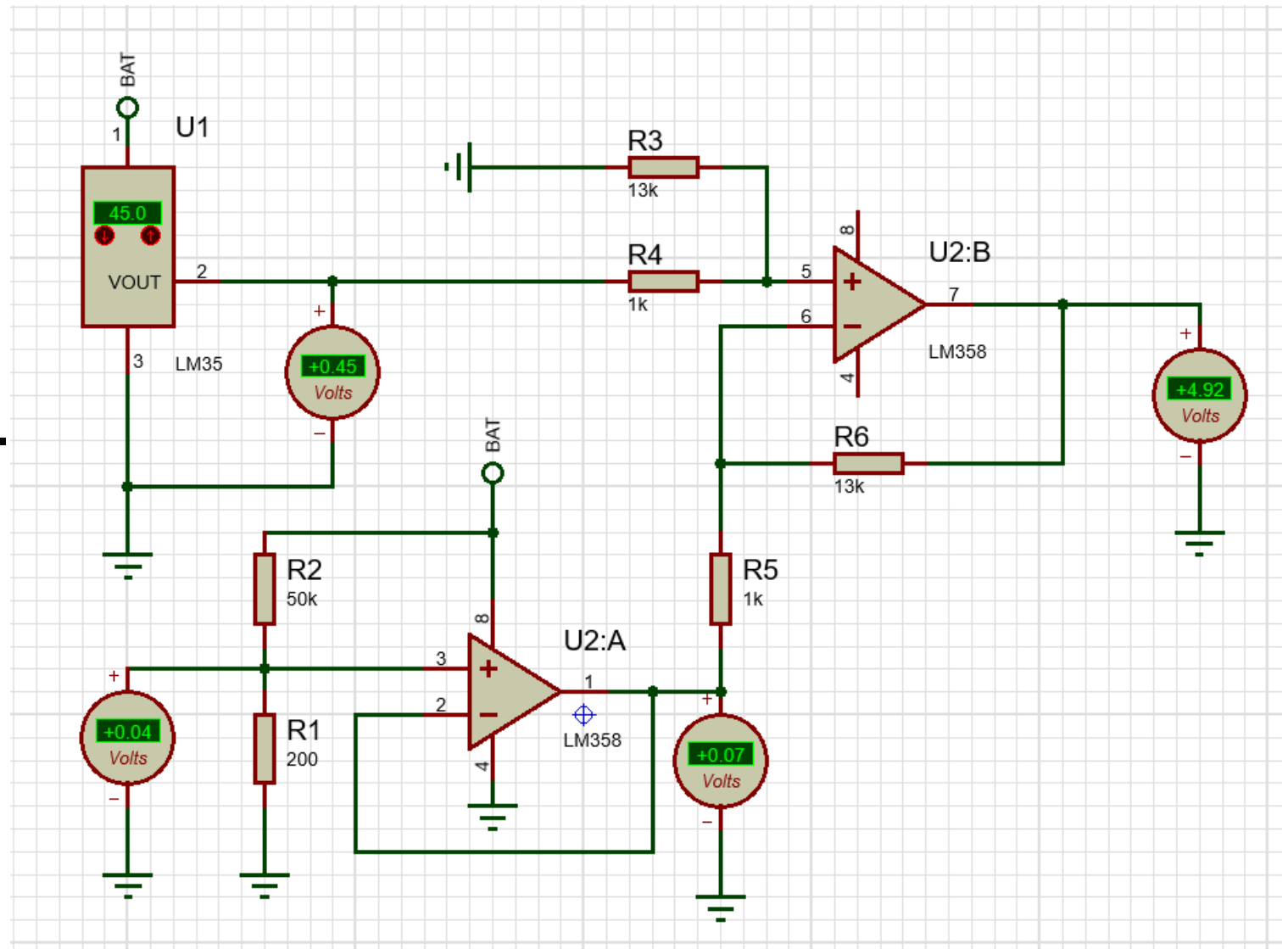
- 450 mV \rightarrow 5V (Gain of differential amplifier)




$$V_{\text{bat}} = 12\text{V} \text{ (why changed?)}$$

Improving Sensor Range

Case Study

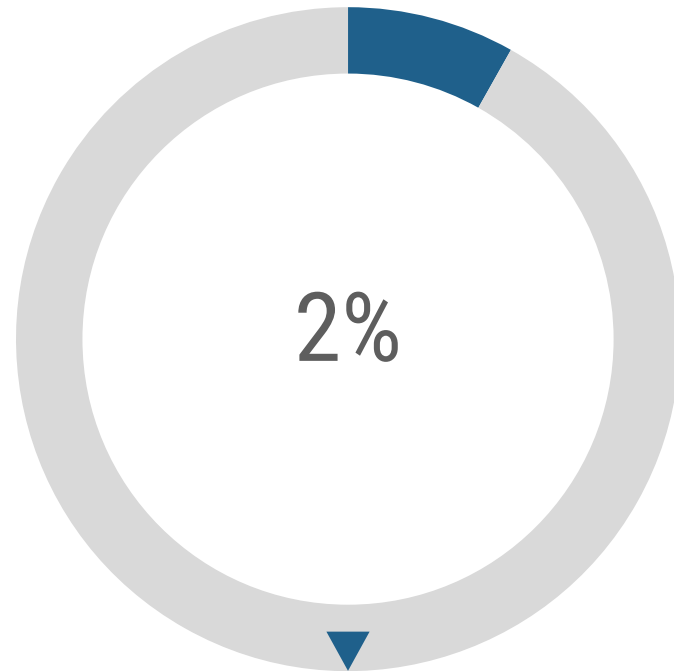

BEFORE

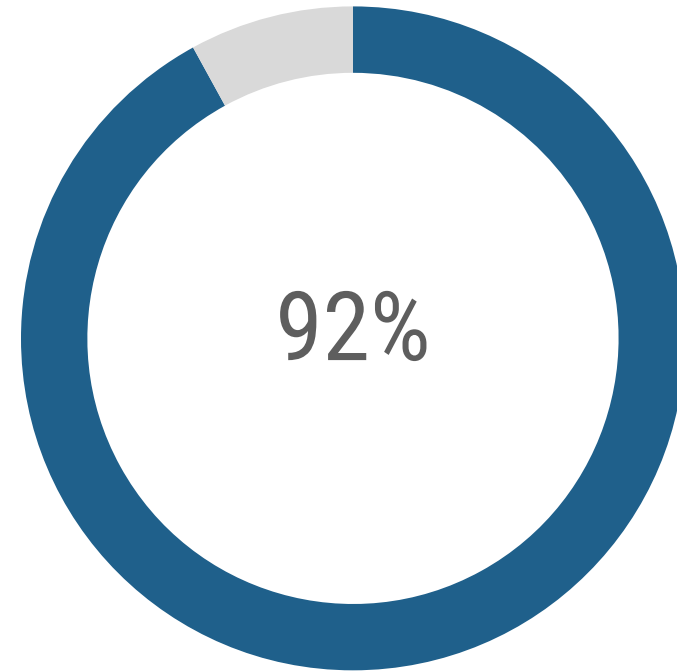

AFTER

Improving Sensor Range

Case Study

PROBLEM DEFINITION

- You wish to build an embedded system for monitoring **temperature** using LM35.
- Your temperature **range** is expected to vary from **10 – 100 °C**
- You have **built-in 10-bit ADC** with **reference** voltage of **5V**.
- You are **assigned** to **improve the voltage range of LM35** to match ADC input voltage range for the input temperature range

APPLY THE DESIGN IN SIMULATION AND
PRACTICAL CIRCUIT

Improving Sensor Range

Case Study

SOLUTION Steps

1. Get sensor minimum and maximum voltages corresponding to given range

$$T_{min} = 10^{\circ} \rightarrow V_{min} = T * \text{sensor sensitivity} = 10^{\circ} * \frac{10mV}{C} = 0.1 V$$

$$T_{max} = 100^{\circ} \rightarrow V_{max} = T * \text{sensor sensitivity} = 100^{\circ} * \frac{10mV}{C} = 1.0 V$$

$$V_{min} = 0.1 V \quad V_{max} = 1.0 V$$

Improving Sensor Range

Case Study


SOLUTION Steps

2. Remove min voltage offset V_{\min} by subtracting it from the same voltage created by a voltage divider

Desired voltage divider output = $V_{\min} = 0.1\text{ V}$

$$V_o = V_s \frac{R_2}{R_1 + R_2} \rightarrow R_1 = R_2 \left(\frac{V_s}{V_o} - 1 \right) \text{ (Derive it if you like)}$$

$$\text{Assuming } V_s = 10\text{V}, R_2 = 100 \rightarrow R_1 = 100 \left(\frac{10}{0.1} - 1 \right) = 9.9\text{k}$$

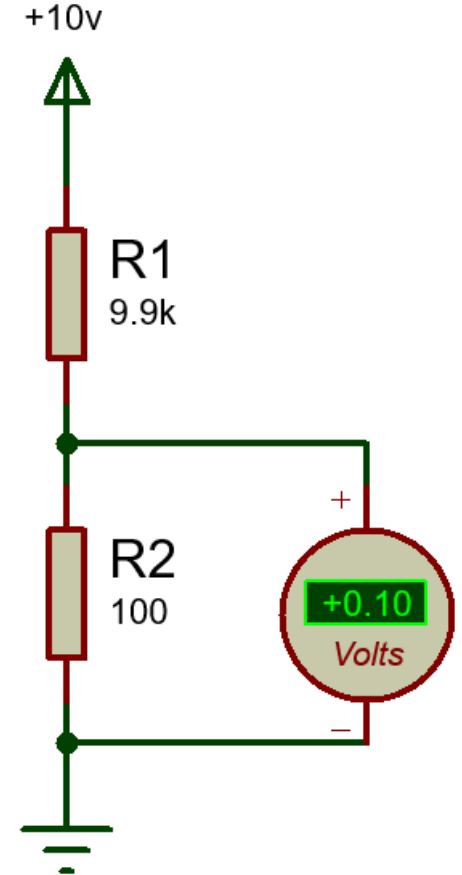


Lab 2

Improving Sensor Range

Case Study

SOLUTION Steps

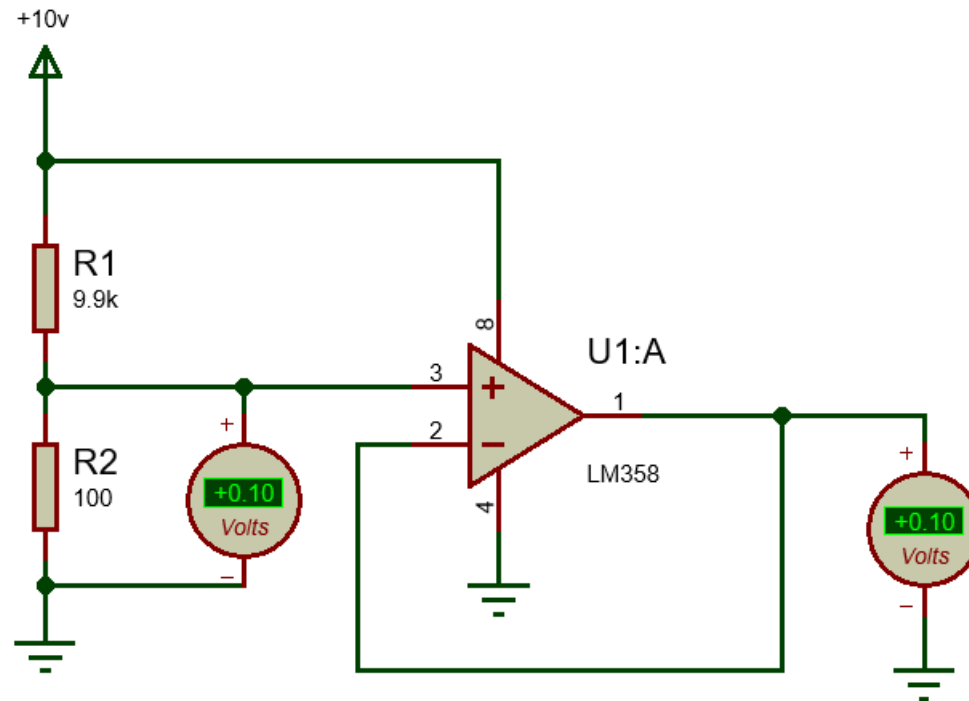3. Apply buffering stage (*as discussed in the lab*)



Improving Sensor Range


Case Study

SOLUTION Steps

- Subtract sensor min and max output voltage from buffer and check new V_{\min} and V_{\max} after subtraction. (use differential amplifier for subtraction with $G = 1$)

$$V_{\min-\text{new}} = 0.1 - 0.1 = 0V$$
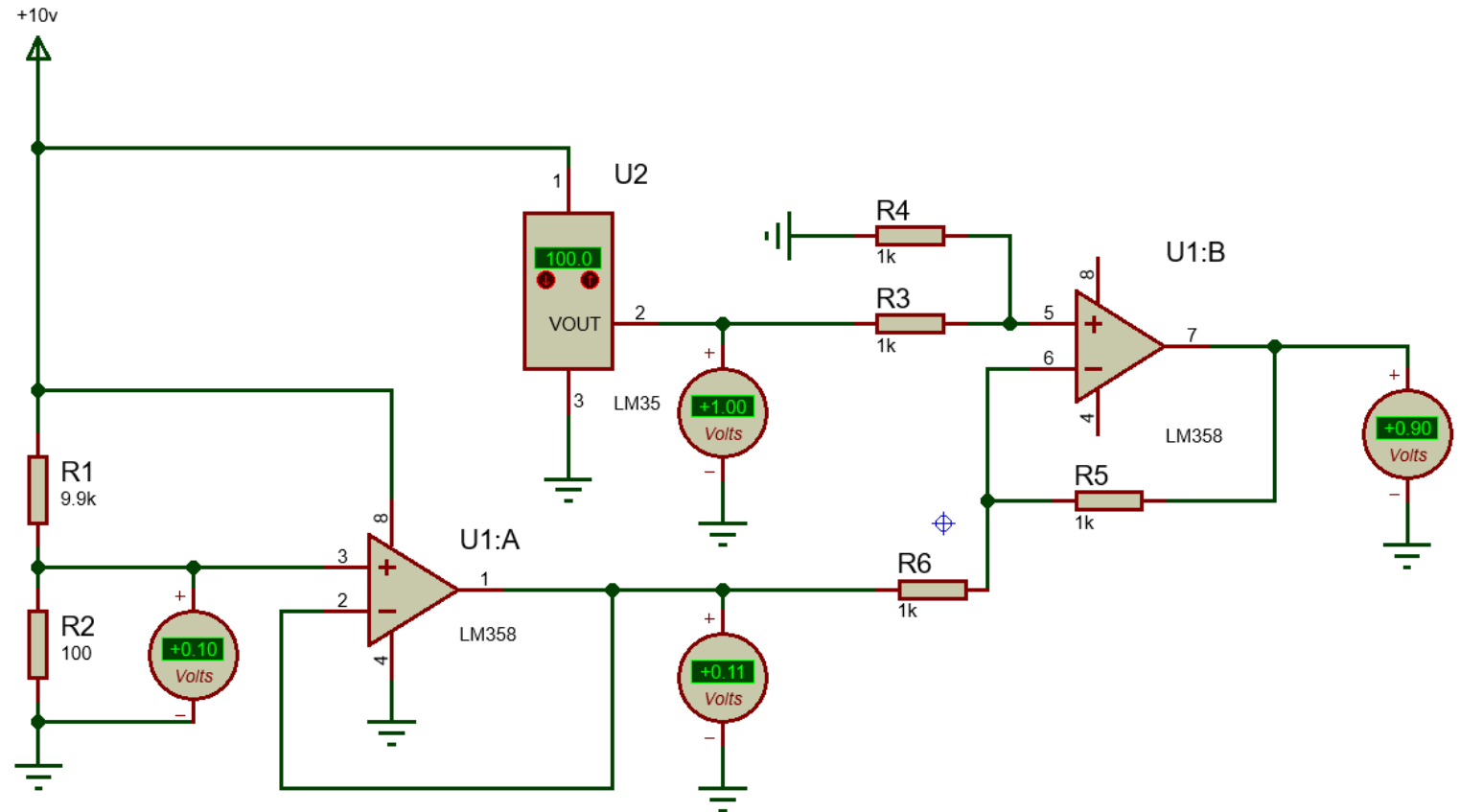
$$V_{\max-\text{new}} = 1.0 - 0.1 = 0.9V$$



Improving Sensor Range

Case Study


SOLUTION Steps

5. To maximize the sensor voltage to ADC V_{ref} , the amplifier gain is set to:

$$G = \frac{V_{ref(ADC)}}{V_{max-new(sensor)}}$$

$$= \frac{5.0}{0.9} = 5.56 \cong 5.5$$

If R_f is $5.5k \rightarrow R_1 = 1k$

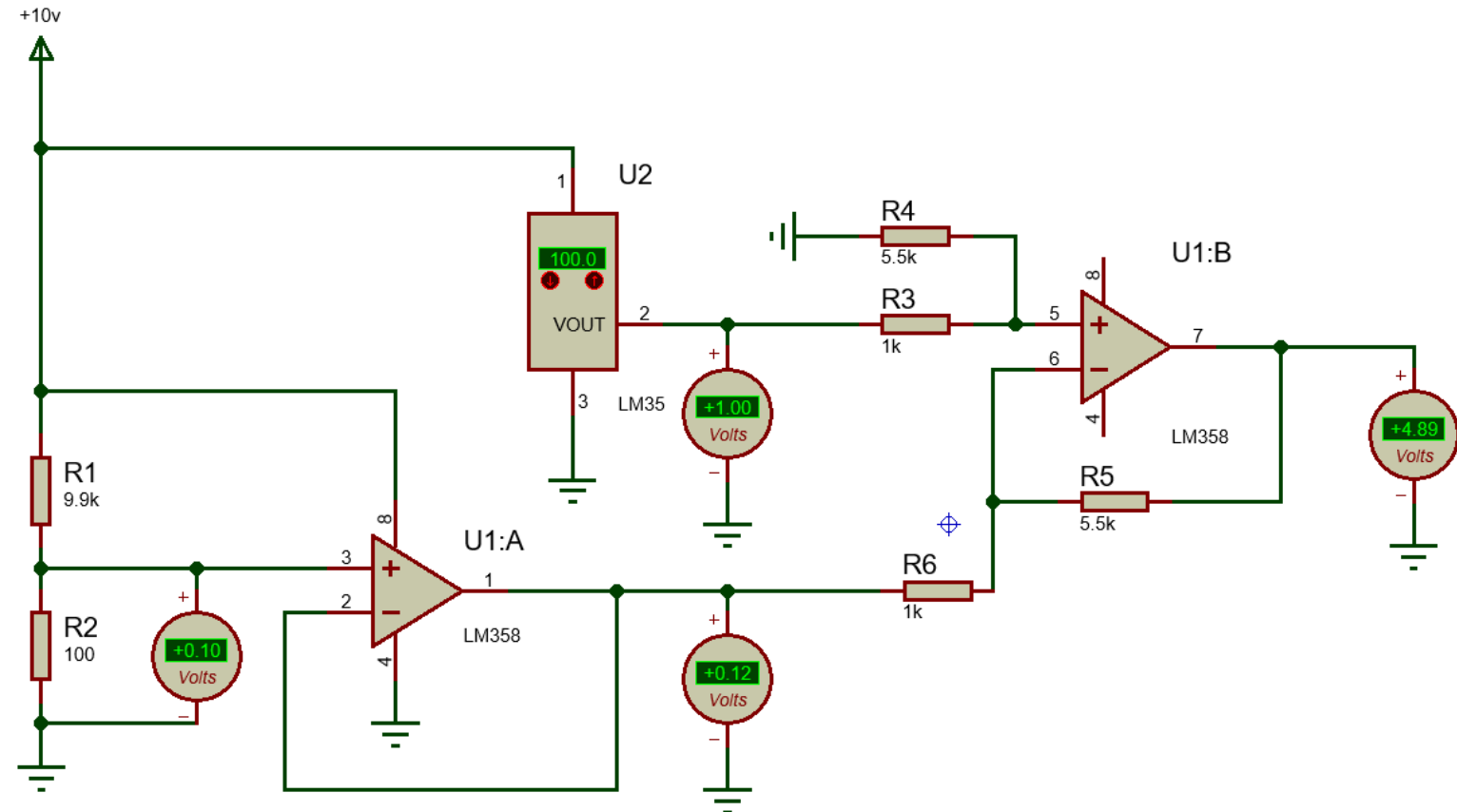

$\therefore @ T = 10^{\circ}C \rightarrow V = (0.1 - 0.1) * 5.5 = 0V$ and $@ T = 100^{\circ}C \rightarrow V = (1.0 - 0.1) * 5.5 = 4.95V$


SENSITIVITY IMPROVEMENT

Before and After

$$\text{Sensor sensitivity} = \frac{10\text{mV}}{^{\circ}\text{C}} \text{ (before signal conditioning)}$$

$$\text{Sensor sensitivity} = \frac{10\text{mV}}{^{\circ}\text{C}} * 5.5 = \frac{55.5\text{mv}}{^{\circ}\text{C}} \text{ (After)}$$

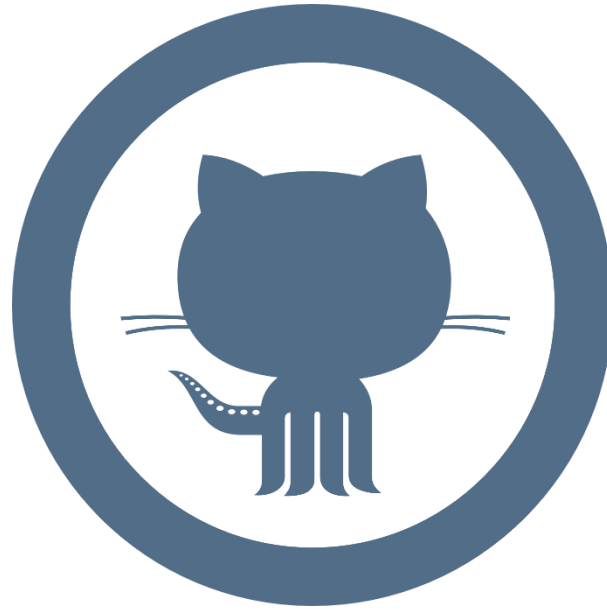*Sensor sensitivity is improved 5.5 times
the original sensitivity*



Don't forget to pull the lab update from.

<http://github.com/wbadry/mte405>

END OF LAB 2